

## 3-PHASE TRANSFORMER TESTS (TR2)

### 5. LOAD CHARACTERISTIC $U_2=f(I_2)$ for p.f.=const

The transformer is supplied from the higher voltage side (Y). The secondary is loaded by a variable 3-phase symmetrical resistor. Connection diagram as in p. 2 with a voltmeter and 3 ammeters added at secondary side. The ranges of meters should correspond to the load test.

During test the supplying voltage should be kept constant and equal to its rated value. The value of  $R_{load}$  should be varied in such a manner as the secondary current value would cover the range (0;  $I_{2N}$ ).

No of read.	$U_1=...$							p.f.=1			
	$I_{1A}$	$I_{1B}$	$I_{1C}$	$I_{2A}$	$I_{2B}$	$I_{2C}$	$U_2$	$I_1$	$I_2$	$\Delta U$	$\eta$
	A	A	A	A	A	A	V	A	A	V	%
1											
2											
3											
...											


$$I_1 = \frac{I_{1A} + I_{1B} + I_{1C}}{3}; \quad I_2 = \frac{I_{2A} + I_{2B} + I_{2C}}{3}; \quad \Delta U = U_{20} - U_2$$

Efficiency value in per-cent can be calculated from the relation:

$$\eta = \frac{P_2}{P_1} \times 100\% = \frac{P_2}{P_2 + \Sigma \Delta P} \times 100\% = \frac{\sqrt{3} U_2 I_2}{\sqrt{3} U_2 I_2 + \left( \frac{I_1}{I_{1N}} \right)^2 P_{CuN} + P_{FeN}} \times 100\%$$

In common coordinates, draw the characteristics:

$$U_2, \Delta U, \eta = f(I_2)$$

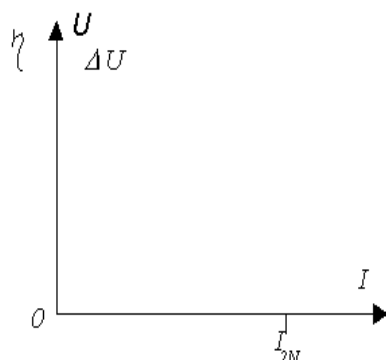

Basing on the results of measurements already performed, calculate per-cent values of the voltage regulation (voltage drop) for the following cases:

- $\Delta U\%$  for  $\cos \varphi_2 = 1$  (compare calculations with measurement results)
- $\Delta U\%$  for  $\cos \varphi_2 = 0.8$  lag.
- $\Delta U\%$  for  $\cos \varphi_2 = 0.5$  lead.


## 6. MEASUREMENT OF VOLTAGE RATIO AND GROUP OF CONNECTIONS

### TEST
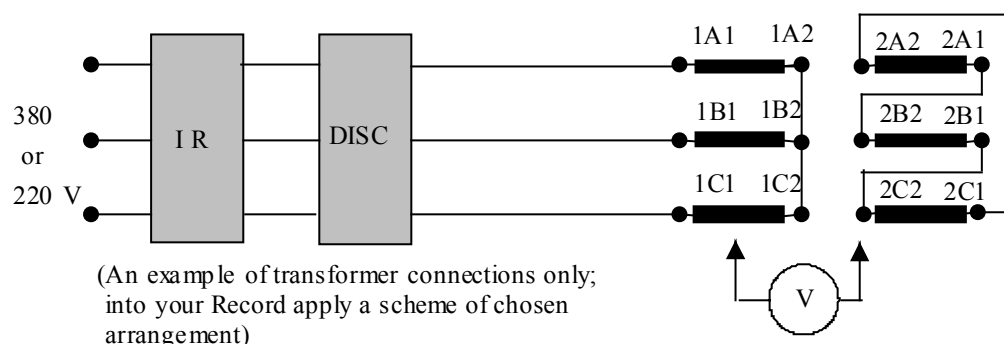
#### 6.1. Voltage ratio

Transformer should be connected into chosen 3-phase arrangement (Yy, Yd, Dy or Dd) and supplied from higher voltage side through induction regulator (IR). By means of the voltmeter do the measurement of corresponding voltages of higher and lower voltage sides for three different values of supplying voltage ( $U_I$  not higher than  $U_N^*$  where  $U_N^*$  is rated voltage for chosen arrangement).

On the basis of determined  $K_{av}$  for chosen and tested arrangement calculate the values of voltage ratios for another possible connections as to have ratios for Yy, Yd, Dy, Dd known.



No of read.	MEASUREMENTS						CALCULATIONS			
	$U_{1A1-1B1}$	$U_{1A1-1C1}$	$U_{1B1-1C1}$	$U_{2A1-2B1}$	$U_{2A1-2C1}$	$U_{2B1-2C1}$	$U_{Iav}$	$U_{2av}$	$K$	$K_{av}$
	V	V	V	V	V	V	V	V	-	-
1										
2										
3										

#### 6.2. Group of connections

Having your transformer connected as in p. 6.1. decide which terminals will be recognised as 1A, 1B, 1C and 2A, 2B, 2C and then connect two terminals 1A and 2A respectively. Supply the transformer with voltage  $U_I=100$  V (or other) and measure the following voltages:

$$\begin{array}{lll}
 U_{1A-1B} = \dots & U_{2A-2B} = \dots & U_{1B-2B} = \dots \\
 U_{1B-2C} = \dots & U_{1C-2B} = \dots & U_{1C-2C} = \dots
 \end{array}$$

At the sheet of drawing paper, applying appropriate scale, draw the triangles (phasor diagrams) of the voltages of higher and lower sides (not forgetting about connection 1A-2A), in order that triangles position confirms measured values of voltages. On the basis of the diagram determine the group of connections.

## **BIBLIOGRAPHY**

1. Fitzgerald A., Kingsley C., Umans S.: *Electric machinery*. McGraw-Hill Book Co. 1985
2. Say M.G.: *Alternating current machines*. Pitman, 1976
3. Nasar S.A., Unnewehr L.E.: *Electromechanics and Electric Machines*. John Wiley, 1979
4. Latek W.: *Teoria maszyn elektrycznych*. WNT, 1987
5. Latek W.: *Badanie maszyn elektrycznych w przemyśle*. WNT, 1987
6. Kamiński G., Kosk J., Przyborowski W.: *Laboratorium maszyn elektrycznych*. Oficyna PW, 2005